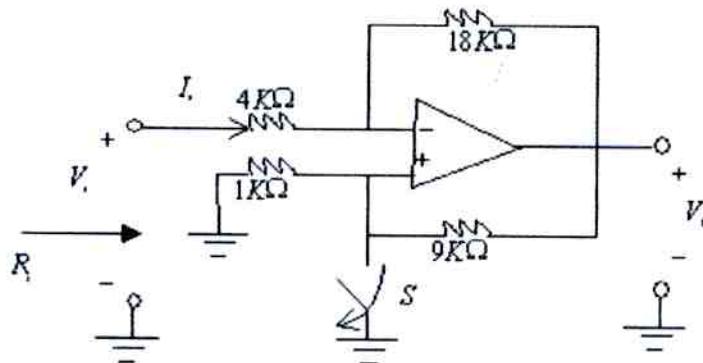


In the operational amplifier circuit shown in the figure, the switch s is closed first. Open the switch s and calculate the voltage gain V_o/V_i . Assume ideal Op-Amp.



a.

$$V_o/V_i = -0.5$$

b.

$$V_o/V_i = -10$$

c.

$$V_o/V_i = -15$$

d.

$$V_o/V_i = -0.1$$