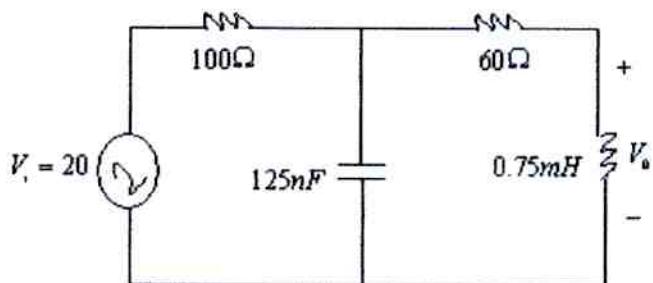


In the RLC circuit shown in the figure, use phasor analysis to find the expression for $v_o(t)$ if $V_i(t) = 20\cos(16E04*t)$ V.



a.

$$v_o(t) = 0.67 \cos(5 * 10^4 t - 11.73) \text{ V}$$

b.

$$v_o(t) = -5.67 \cos(5 * 10^4 t - 11.73) \text{ V}$$

c.

$$v_o(t) = 9.49 \cos(16 * 10^4 t - 18.43) \text{ V}$$

d.

$$v_o(t) = -19.49 \cos(16 * 10^4 t - 18.43) \text{ V}$$