

#12

EC

Ans 11.14 *
11.15

Chge 5

$V_m = 2400$

A 2,400 V, balanced, three-phase delta circuit (see Figure 5-44, page 232 in the textbook) has phase load impedances of $40+j60$ OHMS. Find the line currents I_{aA} , I_{bB} , and I_{cC} .

NOTE: Just as the current I_{aA} shown in Figure 5.44 is the current flowing from node a to node A, the current I_{bB} is the current flowing from node b to node B, and the current I_{cC} is the current flowing from node c to node C.

a. $I_{aA} = 57.64 e^{j86.3^\circ}$, $I_{bB} = 57.64 e^{-j153.7^\circ}$, $I_{cC} = 57.64 e^{-j33.7^\circ}$

b. $I_{aA} = 33.28 e^{-j56.3^\circ}$, $I_{bB} = 33.28 e^{-j176.3^\circ}$, $I_{cC} = 33.28 e^{j63.7^\circ}$

c. $I_{aA} = 57.64 e^{-j86.3^\circ}$, $I_{bB} = 57.64 e^{j153.7^\circ}$, $I_{cC} = 57.64 e^{j33.7^\circ}$

d. $I_{aA} = 33.28 e^{j56.3^\circ}$, $I_{bB} = 33.28 e^{j176.3^\circ}$, $I_{cC} = 33.28 e^{-j63.7^\circ}$

$Z_{\Delta} = 40 + j60 \Rightarrow 72.1 \angle 56.3^\circ$

$V_L = 2400$

$V_{\phi} = 2400 \angle -30^\circ$

$V_{\phi} = 2400 \angle -90^\circ$

$V_{\phi} = 2400 \angle 150^\circ$

$I_{\Delta} = \frac{V_{\phi}}{Z_{\Delta}} = \frac{2400}{72.1 \angle 56.3^\circ} = 33.28 \angle -86.3^\circ$

$I_{\Delta} = \frac{2400}{72.1 \angle 56.3^\circ}$

$48 \angle -30^\circ$

$I_{AC} = I_{\Delta} \angle$