


#16

- Charge

Consider the following circuit. The voltage step is an "ideal" pulse going from 0 V TO 4 V and then back to 0 V; The pulse width is 5 microseconds wide.

What is the voltage across the resistor, $v_R(t)$, 7 microseconds after the rising edge of the input pulse?

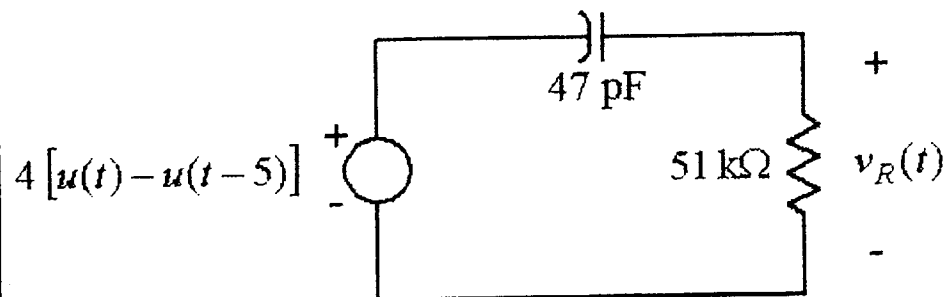Note : {Time measures in μs (microseconds)}



- between 0.1 V and 1 V
- between 0 V and -1 V
- between 1.1 V and 2 V
- between -1.1 V and -2 V