

(23) Conservation of energy requires that the sum of the power absorbed by all the elements in a circuit be zero. The following figure shows a circuit. All of the element voltage and current are specified. Are these voltages and currents correct?
 Hint: Calculate the power absorbed by each element and add them up.

