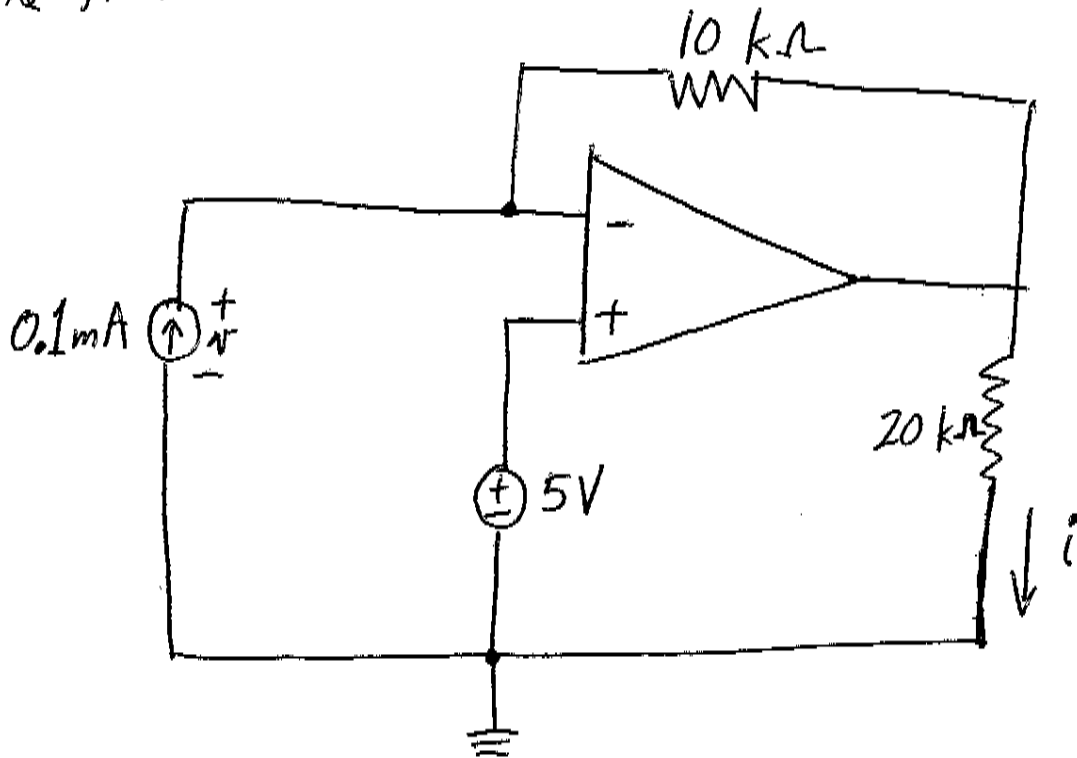


12.13 Find v and i for the circuit shown. Assume an ideal op amp. Please show how you arrived at your answer, and why the final answer is a positive or negative.



$v =$

- a) $-5V$
- b) $-4V$
- c) $+4V$
- d) $+5V$

$i =$

- a) -0.25 ma
- b) -0.2 ma
- c) $+0.1\text{ ma}$
- d) $+0.2\text{ ma}$