
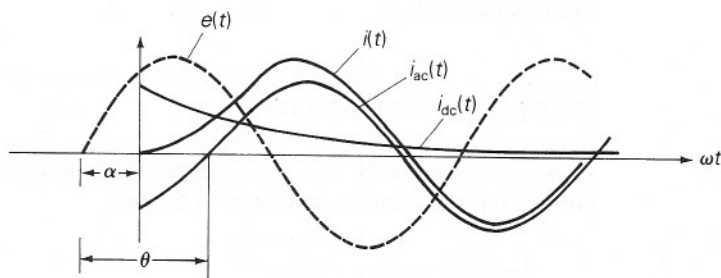


FIGURE 7.1

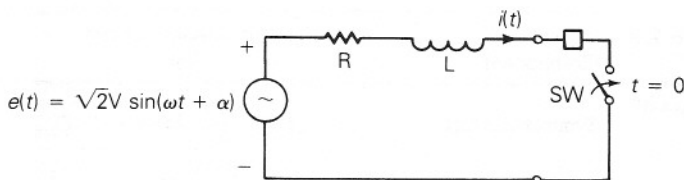in a series R-L  
with ac voltage  
source



$$i_{ac}(t) = \frac{\sqrt{2}V}{Z} \sin(\omega t + \alpha - \theta) \quad \text{A} \quad (7.1.3)$$

$$i_{dc}(t) = -\frac{\sqrt{2}V}{Z} \sin(\alpha - \theta)e^{-t/T} \quad \text{A} \quad (7.1.4)$$

$$Z = \sqrt{R^2 + (\omega L)^2} = \sqrt{R^2 + X^2} \quad \Omega \quad (7.1.5)$$

$$\theta = \tan^{-1} \frac{\omega L}{R} = \tan^{-1} \frac{X}{R} \quad (7.1.6)$$

$$T = \frac{L}{R} = \frac{X}{\omega R} = \frac{X}{2\pi f R} \quad \text{s} \quad (7.1.7)$$

The total fault current in (7.1.2), called the *asymmetrical fault current*, is plotted in Figure 7.1 along with its two components. The ac fault current (also called *symmetrical* or *steady-state fault current*), given by (7.1.3), is a sinusoid. The *dc offset current*, given by (7.1.4), decays exponentially with time constant  $T = L/R$ .

The rms ac fault current is  $I_{ac} = V/Z$ . The magnitude of the dc offset, which depends on  $\alpha$ , varies from 0 when  $\alpha = \theta$  to  $\sqrt{2}I_{ac}$  when  $\alpha = (\theta \pm \pi/2)$ . Note that a short circuit may occur at any instant during a cycle of the ac source; that is,  $\alpha$  can have any value. Since we are primarily interested in the largest fault current, we choose  $\alpha = (\theta - \pi/2)$ . Then (7.1.2) becomes

$$i(t) = \sqrt{2}I_{ac}[\sin(\omega t - \pi/2) + e^{-t/T}] \quad \text{A} \quad (7.1.8)$$

where

$$I_{ac} = \frac{V}{Z} \quad \text{A} \quad (7.1.9)$$

The rms value of  $i(t)$  is of interest. Since  $i(t)$  in (7.1.8) is not strictly periodic, its rms value is not strictly defined. However, treating the exponential term as