

Two balanced, in-parallel connected, three-phase loads are fed by a three-phase line with an impedance of  $(2+j4) \Omega$  per phase. The first load is  $\Delta$ -connected with an impedance of  $(60 + j45) \Omega$  per phase, and the second load is Y-connected with an impedance of  $(30 + j40) \Omega$  per phase. The line is energized at the sending end from a 60-Hz, three-phase balanced voltage source with line-to-line voltage of  $120\sqrt{3} V$  rms. Given the phase voltage and the per-phase current delivered by the source as:

$\bar{V}_1 = 120 V$  and  $\bar{I} = 5 \angle 0^\circ$  correspondingly, calculate the line voltage at the load.

a.

$$V_{LOAD(\Delta-Y-\Delta)} = 183.64 V$$

b.

$$V_{LOAD(\Delta-Y-\Delta)} = 293.64 V$$

c.

$$V_{LOAD(\Delta-Y-\Delta)} = 193.64 V$$

d.

$$V_{LOAD(\Delta-Y-\Delta)} = 103.64 V$$