

Two balanced, in-parallel connected, three-phase loads are fed by a three-phase line with an impedance of $(2+j4) \Omega$ per phase. The first load is Δ -connected with an impedance of $(60 + j45) \Omega$ per phase, and the second load is Y-connected with an impedance of $(30 + j40) \Omega$ per phase. The line is energized at the sending end from a 60-Hz, three-phase balanced voltage source with line-to-line voltage of $120\sqrt{3} V$ rms. The phase voltage and the per-phase current delivered by the source are given as:

$\bar{V}_1 = 120 V$ and $I = 5 \angle 0^\circ$ correspondingly. Calculate the total three-phase real and reactive power absorbed by each load, and the total three-phase real and reactive power absorbed by the line.

- $\bar{S}_1 = 450 W + j600 VAR, \bar{S}_2 = 1200 W - j900 VAR, \bar{S}_{LINE} = 150 W + j300 VAR,$
- $\bar{S}_1 = 450 W + j600 VAR, \bar{S}_2 = 1800 W - j900 VAR, \bar{S}_{LINE} = 150 W + j800 VAR,$
- $\bar{S}_1 = 450 W + j600 VAR, \bar{S}_2 = 1200 W - j900 VAR, \bar{S}_{LINE} = 180 W + j500 VAR,$
- $\bar{S}_1 = 150 W + j400 VAR, \bar{S}_2 = 1200 W - j900 VAR, \bar{S}_{LINE} = 150 W - j300 VAR,$