

4. For the logic circuit shown in Fig. 3, determine F in terms A, B and C. Simplify the resulting expression so it has the fewest terms containing only NAND. Then check the simplified expression with the original by constructing a truth table.

