

Consider the circuit below. Determine the range of resistor (R) values for which the following two conditions will be true:

$$V \geq 15 \text{ V}$$

$$P_R \geq 5 \text{ W}$$

Express your final answer to the nearest Ω .

Resistor Range: _____

