

The voltage and current at the terminals of the circuit element in Fig. 1.5 are zero for $t < 0$. For $t \geq 0$ they are

$$v = 80,000te^{-500t} \text{ V}, \quad t \geq 0;$$

$$i = 15te^{-500t} \text{ A}, \quad t \geq 0.$$

- Find the time (in milliseconds) when the power delivered to the circuit element is maximum.
- Find the maximum value of p in milliwatts.
- Find the total energy delivered to the circuit element in microjoules.

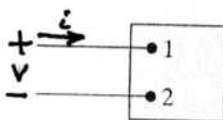


Figure 1.5 An ideal basic circuit element.