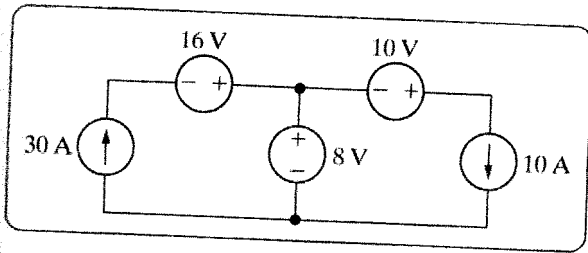


If the interconnection in Fig. P2.7 is valid, find the power developed by the current sources. If the interconnection is not valid, explain why.

Figure P2.7



If the interconnection in Fig. P2.8 is valid, find the total power developed in the circuit. If the interconnection is not valid, explain why.