

- a) Is the interconnection in Fig. P2.12 valid? Explain.
- b) Can you find the total energy developed in the circuit? Explain.

Figure P2.12

