

Find (a) i_o , (b) i_1 , and (c) i_2 in the circuit in Fig. P2.28.

Figure P2.28

