

2.21 The voltage and current were measured at the terminals of the device shown in Fig. P2.21(a). The results are tabulated in Fig. P2.21(b).

- Construct a circuit model for this device using an ideal voltage source and a resistor.
- Use the model to predict the amount of power the device will deliver to a $40\ \Omega$ resistor.

Figure P2.21

