

- 2.15 The current  $i_a$  in the circuit shown in Fig. P2.15 is 20 A. Find (a)  $i_o$ ; (b)  $i_g$ ; and (c) the power delivered by the independent current source.

**P**

Figure P2.15

