

2.23 The table in Fig. P2.23(a) gives the relationship between the terminal voltage and current of the practical constant voltage source shown in Fig. P2.23(b).

- Plot v_s versus i_s .
- Construct a circuit model of the practical source that is valid for $0 \leq i_s \leq 24$ A, based on the equation of the line plotted in (a). (Use an ideal voltage source in series with an ideal resistor.)
- Use your circuit model to predict the current delivered to a $1\ \Omega$ resistor connected to the terminals of the practical source.
- Use your circuit model to predict the current delivered to a short circuit connected to the terminals of the practical source.

- What is the actual short-circuit current?
- Explain why the answers to (d) and (e) are not the same.

Figure P2.23

