

2.14 Given the circuit shown in Fig. P2.14, find

- P
- a) the value of i_a ,
 - b) the value of i_b ,
 - c) the value of v_o ,
 - d) the power dissipated in each resistor,
 - e) the power delivered by the 200 V source.

Figure P2.14

