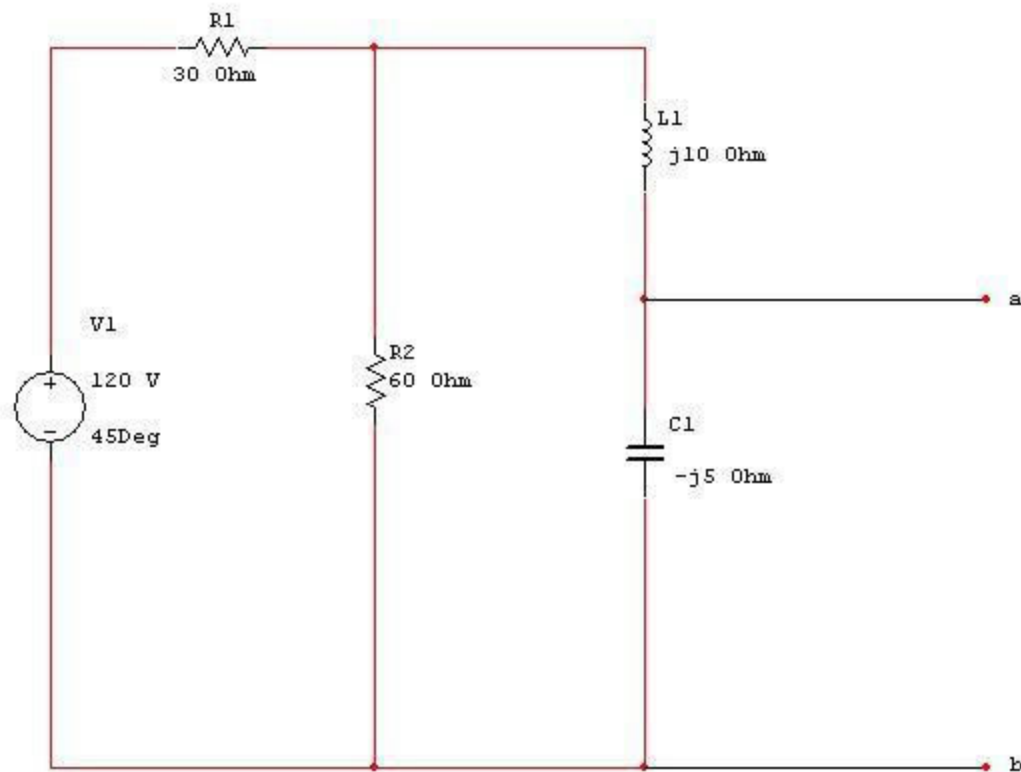


For the circuit shown below, calculate the Norton equivalent circuit at terminals a-b.



a.  $I_{sc} = 1.258 \angle -28.13^\circ$  A

b.  $I_{sc} = 3.578 \angle 18.43^\circ$  A

c.  $I_{sc} = 2.258 \angle -23.13^\circ$  A

d.  $I_{sc} = 1.428 \angle -13.63^\circ$  A