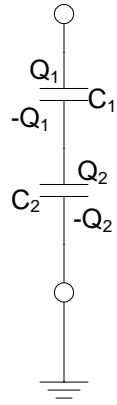


1) Two capacitors in series, calculate the ratio of stored energy.



2) Calculate this ratio for capacitors connected in parallel:

