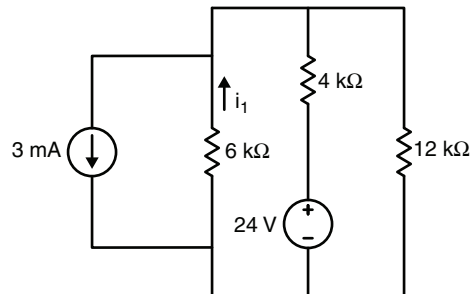


**Issued:** Tuesday, March 6, 2007

**Due:** Tuesday, March 13, 2007

**Reading:** Mayergoyz and Lawson §6.2–6.5


**Problem 6.1**



- (a) Use the method of superposition to determine the current  $i_1$  in the above circuit.
- (b) Now solve for  $i_1$  using the node-voltage method, and show that you get the same result.
- (c) Based on your answer to (a) and (b), calculate how much power is dissipated in each of the three resistors in the circuit.
- (d) Calculate how much power the voltage source is supplying/consuming.
- (e) Calculate how much power the current source is supplying/consuming.

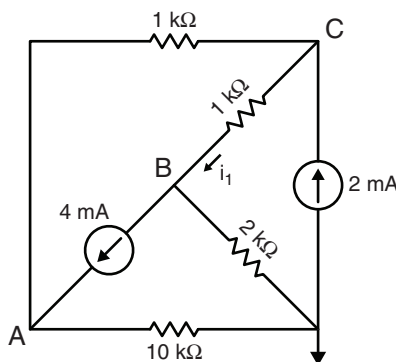**Problem 6.2**

In the following circuit, the nodes have been labeled for you and a reference node has been selected.



- (a) Use the node-voltage method to derive a set of linear equations that could be used to solve for the unknown node voltages  $v_A$ ,  $v_B$  and  $v_C$  in the above figure.


Collect your equations into a matrix equation of the form:  $\mathbf{Ax} = \mathbf{b}$  where

$$\mathbf{x} \equiv \begin{bmatrix} v_A \\ v_B \\ v_C \end{bmatrix}$$

- (b) Solve the equations to obtain the node voltages. (You may use Matlab, your calculator, or other tools, but please check your result to make sure that it is self-consistent.)
- (c) Determine the current  $i_1$ .

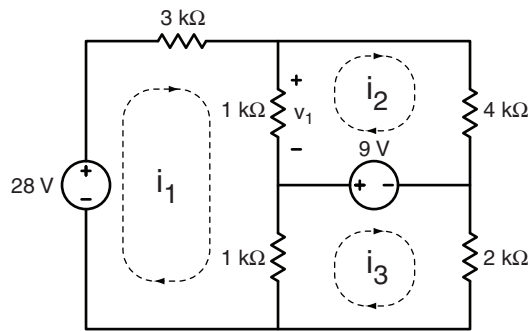**Problem 6.3**

In the following circuit, the mesh-currents have been labeled for you.




- (a) Use the mesh-current method to derive a set of linear equations that could be used to solve for the unknown mesh-currents  $i_1$ ,  $i_2$  and  $i_3$  in the above figure. Collect your equations into a matrix equation of the form:  $\mathbf{Ax} = \mathbf{b}$  where

$$\mathbf{x} \equiv \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix}$$

- (b) Solve the equations to obtain the currents. (You may use Matlab, your calculator, or other tools, but please check your result to make sure that it is self-consistent.)
- (c) Determine the voltage  $v_1$ .

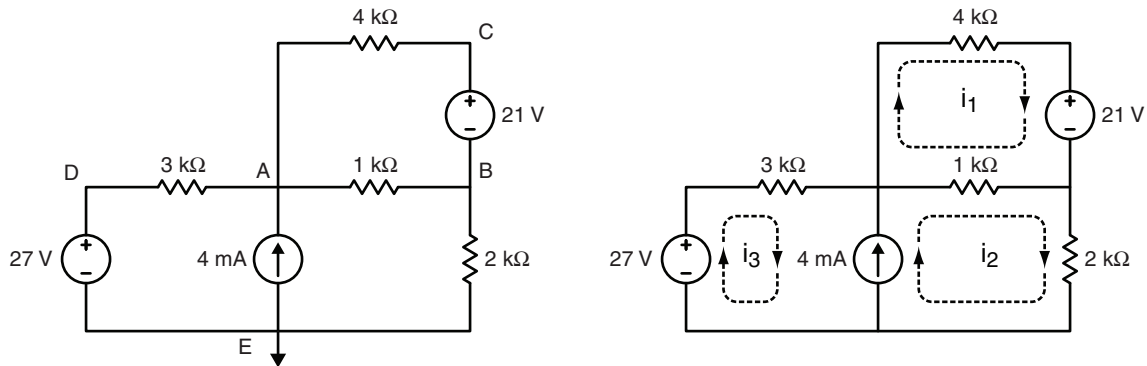**Problem 6.4**

The following circuit can be solved using either the node-voltage or mesh-current method.



- (a) Use the node-voltage method to derive a set of linear equations that can be used to solve for the two unknown node voltages  $v_A$  and  $v_B$  in the above figure. Collect your equations into a matrix equation of the form:  $\mathbf{Ax} = \mathbf{b}$  where

$$\mathbf{x} \equiv \begin{bmatrix} v_A \\ v_B \end{bmatrix}$$


- (b) Now use the mesh-current analysis to derive a set of linear equations that can be used to solve for the mesh currents  $i_1$  and  $i_2$  in the same circuit. Collect your equations into a matrix equation of the form:  $\mathbf{Ax} = \mathbf{b}$  where

$$\mathbf{x} \equiv \begin{bmatrix} i_1 \\ i_2 \end{bmatrix}$$

- (c) Solve for all of the unknown currents and voltages using either technique. You may use a calculator to check your answers, but you must solve the equations by hand and show work. Draw a large copy of the circuit and clearly indicate the values for all of the branch voltages and currents.

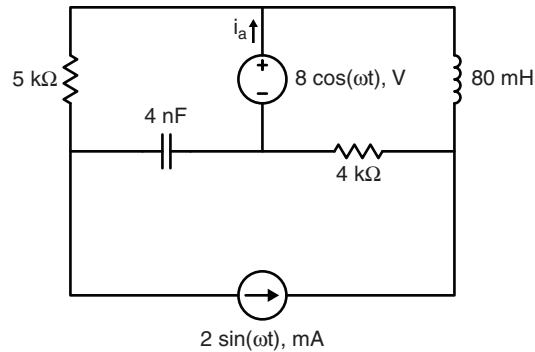**Problem 6.5**


The following circuit is operating in the AC steady state, with an angular frequency of  $\omega = 50$  krad/s.



Solve this circuit using either the node-voltage or mesh-current method. Then answer the following questions:

- (a) Determine  $\hat{I}_a$ , the complex phasor that represents the current flowing through the voltage source. Please express your answer in rectangular ( $a + jb$ ) coordinates.
- (b) Determine the time-averaged power supplied by the voltage source.
- (c) Determine the time-averaged power supplied by the current source.
- (d) Determine the time-averaged power consumed by the 4 kΩ and 5 kΩ resistors. Then using your answers from (b)... (d) verify that the total power is conserved.

**Problem 6.6**

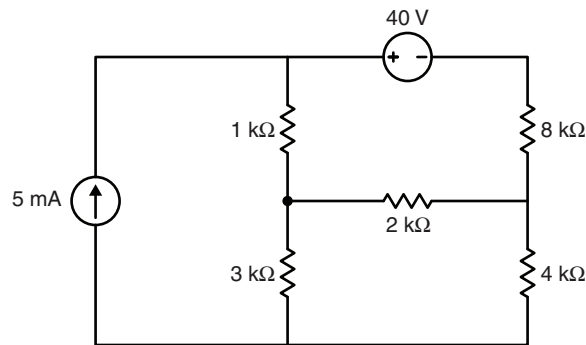

Calculate all of the unknown voltages and currents in the above circuit, using either the node-voltage, mesh-current, or superposition method (your choice.) Mark your answers directly on a copy of the circuit. In all cases, label the *actual* direction of current flow and the true polarity of the voltages (i.e., none of your indicated quantities should be negative.)