

2.16

P

- Find the currents  $i_g$  and  $i_o$  in the circuit in Fig. P2.16.
- Find the voltage  $v_o$ .
- Verify that the total power developed equals the total power dissipated.

Figure P2.16

