

11.4

A lossless transmission line having $Z_0 = 120 \Omega$ is operating at $\omega = 5 \times 10^8$ rad/s. If the velocity on the line is 2.4×10^8 m/s, find: (a) L ; (b) C .
(c) Let Z_L be represented by an inductance of $0.6 \mu\text{H}$ in series with a 100Ω resistance. Find Γ and s .