

Use Smith chart

- 11.36** The two-wire lines shown in Figure 11.36 are all lossless and have $Z_0 = 200 \Omega$. Find d and the shortest possible value for d_1 to provide a matched load if $\lambda = 100$ cm.

